
EE2003: Computer Organisation

Assignment # 2

By :

Anchal Debnath

(EE21B017)

Question 22

Design a 16-bit Kogge-Stone prefix adder module in Verilog. The module should take two 16-bit inputs (A and B) and produce a 16-bit output Sum

Date:

1st October 2023

Contents

0.1	About Kogge Stone Adder	ii
1	Verilog Code	iv
1.0.1	Verilog Design Code	iv
1.0.2	Verilog Testbench Code	vi
2	Outputs	viii
3	References	viii

0.1 About Kogge Stone Adder

 


Figure 1: 16 bit Kogge stone Adder Schematic 1

A 16-bit Kogge-Stone adder is a high-performance digital circuit used for adding two 16-bit binary numbers efficiently. It relies on a parallel prefix tree structure to compute the addition result with minimal delay. Here's how the mechanism of a 16-bit Kogge-Stone adder works:

1. Input Signals: - A[15:0] and B[15:0]: The two 16-bit binary numbers to be added. - Cin: The input carry bit, which is typically set to zero for the first stage of the adder.

2. Generation of Generate (g) and Propagate (p) Signals: - For each bit position from the least significant bit (LSB) to the most significant bit (MSB): - g[i] (Generate Signal): Indicates whether a carry will be generated at bit position i if there is a carry-in at this position. It is calculated as $g[i] = A[i] \text{ and } B[i]$. - p[i] (Propagate Signal): Indicates whether a carry from the previous bit position will propagate to bit position i. It is calculated as $p[i] = A[i] \text{ xor } B[i]$.

$$\begin{aligned}
 P_{i:j} &= P_{i:k} P_{k-1:j} \\
 G_{i:j} &= G_{i:k} + P_{i:k} G_{k-1:j} \\
 G_{-1} &= C_{in}
 \end{aligned}$$

3. Parallel Prefix Tree Structure: - The Kogge-Stone adder employs a tree-like structure to efficiently compute the carry signals and the sum outputs in parallel. - The tree structure consists of multiple levels, with each level processing a different set of bits. Level 0 handles the LSB, and each subsequent level processes additional bits.

4. Carry Computation in Each Level: - At each level of the tree, the generate (g) and propagate (p) signals are used to calculate the carry-out (Cout) and carry-in (Cin)

for the next level. - The carry-out (Cout) for each bit position is determined by the OR operation on the generate signal of the current bit and the AND operation between the propagate signal of the current bit and the carry-in (Cin) from the previous bit. This can be expressed as: - $Cout[i] = g[i] \text{ or } (p[i] \text{ and } Cin)$

5. Sum Calculation: - The sum bit for each position is calculated by XORing the propagate signal of the current bit with the carry-in (Cin). This can be expressed as: - $Sum[i] = p[i] \oplus Cin$

6. Output Carry (Cout): - The carry-out (Cout) of the most significant bit (MSB) represents the overall carry-out from the addition. It is directly taken as the output carry (Cout) of the adder.

7. Output Sum: - The sum bits (Sum[15:0]) represent the result of the addition of the two 16-bit binary numbers.

8. Final Output: - The final output consists of the 16-bit sum (Sum[15:0]) and the output carry (Cout), which can be used to detect overflow.

By employing this parallel prefix tree structure, the 16-bit Kogge-Stone adder can efficiently add two 16-bit binary numbers in a single clock cycle while minimizing the critical path delay, making it suitable for high-speed arithmetic operations in digital circuits.

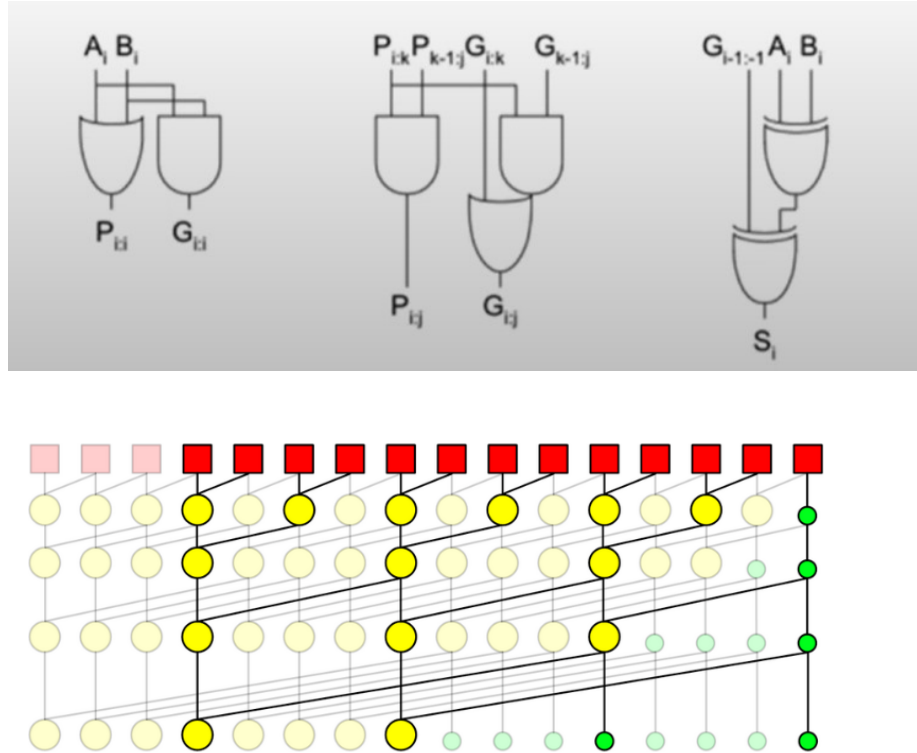


Figure 2: 16 bit Kogge stone Adder Schematic 1

1 Verilog Code

I used EDA Playground (an online simulator) for the code compilation and simulation.

1.0.1 Verilog Design Code

```
1 // 16 bit Kogge Stone Adder
2 module and2(input wire i0,i1, output wire o);
3     assign o = i0 & i1;
4 endmodule
5
6 module or2(input wire i0, i1, output wire o);
7     assign o = i0 | i1;
8 endmodule
9
10 module xor2 (input wire i0,i1, output wire o);
11     assign o = i0 ^ i1;
12 endmodule
13
14 module pro_gen1(input wire x,y, output wire g,p);
15     xor2 o(x,y,p);
16     and2 a(x,y,g);
17 endmodule
18
19 module gen(input wire p10,g00,g10,output wire g11);
20     wire temp;
21     and2 a(g00,p10,temp);
22     or2 o(g10,temp,g11);
23 endmodule
24
25 module pro_gen2(input wire p00,p10,g00,g10, output wire p11,g11);
26     wire tem;
27     and2 a1(p00,p10,p11);
28     and2 a2(g00,p10,tem);
29     or2 o1(tem,g10,g11);
30 endmodule
31
32 module sum(input wire x,y, output wire s);
33     xor2 xor1(x,y,s);
34 endmodule
35
36 module koggestone16(input wire [15:0] A,B,input wire Cin,output
37     wire [15:0] Sum,cout);
38     wire p0[15:0],g0[15:0];
39     wire p1[15:2],g1[15:1];
40     wire p2[15:4],g2[15:2];
41     wire p3[15:8],g3[15:4];
42     wire g4[15:8];
43
44     //0 level
45     pro_gen1 Prop0(A[0],B[0],g0[0],p0[0]);
46     pro_gen1 Prop1(A[1],B[1],g0[1],p0[1]);
```

```

46 pro_gen1 Prop2(A[2],B[2],g0[2],p0[2]);
47 pro_gen1 Prop3(A[3],B[3],g0[3],p0[3]);
48 pro_gen1 Prop4(A[4],B[4],g0[4],p0[4]);
49 pro_gen1 Prop5(A[5],B[5],g0[5],p0[5]);
50 pro_gen1 Prop6(A[6],B[6],g0[6],p0[6]);
51 pro_gen1 Prop7(A[7],B[7],g0[7],p0[7]);
52 pro_gen1 Prop8(A[8],B[8],g0[8],p0[8]);
53 pro_gen1 Prop9(A[9],B[9],g0[9],p0[9]);
54 pro_gen1 Prop10(A[10],B[10],g0[10],p0[10]);
55 pro_gen1 Prop11(A[11],B[11],g0[11],p0[11]);
56 pro_gen1 Prop12(A[12],B[12],g0[12],p0[12]);
57 pro_gen1 Prop13(A[13],B[13],g0[13],p0[13]);
58 pro_gen1 Prop14(A[14],B[14],g0[14],p0[14]);
59 pro_gen1 Prop15(A[15],B[15],g0[15],p0[15]);
60
61
62 // 1 level
63 gen pro1(p0[1],g0[0],g0[1],g1[1]);
64 pro_gen2 pro2(p0[1],p0[2],g0[1],g0[2],p1[2],g1[2]);
65 pro_gen2 pro3(p0[2],p0[3],g0[2],g0[3],p1[3],g1[3]);
66 pro_gen2 pro4(p0[3],p0[4],g0[3],g0[4],p1[4],g1[4]);
67 pro_gen2 pro5(p0[4],p0[5],g0[4],g0[5],p1[5],g1[5]);
68 pro_gen2 pro6(p0[5],p0[6],g0[5],g0[6],p1[6],g1[6]);
69 pro_gen2 pro7(p0[6],p0[7],g0[6],g0[7],p1[7],g1[7]);
70 pro_gen2 pro8(p0[7],p0[8],g0[7],g0[8],p1[8],g1[8]);
71 pro_gen2 pro9(p0[8],p0[9],g0[8],g0[9],p1[9],g1[9]);
72 pro_gen2 pro10(p0[9],p0[10],g0[9],g0[10],p1[10],g1[10]);
73 pro_gen2 pro11(p0[10],p0[11],g0[10],g0[11],p1[11],g1[11]);
74 pro_gen2 pro12(p0[11],p0[12],g0[11],g0[12],p1[12],g1[12]);
75 pro_gen2 pro13(p0[12],p0[13],g0[12],g0[13],p1[13],g1[13]);
76 pro_gen2 pro14(p0[13],p0[14],g0[13],g0[14],p1[14],g1[14]);
77 pro_gen2 pro15(p0[14],p0[15],g0[14],g0[15],p1[15],g1[15]);
78
79 // 2 level
80 gen prop1(p1[2],g0[0],g1[2],g2[2]);
81 gen prop2(p1[3],g1[1],g1[3],g2[3]);
82 pro_gen2 prop3(p1[2],p1[4],g1[2],g1[4],p2[4],g2[4]);
83 pro_gen2 prop4(p1[3],p1[5],g1[3],g1[5],p2[5],g2[5]);
84 pro_gen2 prop5(p1[4],p1[6],g1[4],g1[6],p2[6],g2[6]);
85 pro_gen2 prop6(p1[5],p1[7],g1[5],g1[7],p2[7],g2[7]);
86 pro_gen2 prop7(p1[6],p1[8],g1[6],g1[8],p2[8],g2[8]);
87 pro_gen2 prop8(p1[7],p1[9],g1[7],g1[9],p2[9],g2[9]);
88 pro_gen2 prop9(p1[8],p1[10],g1[8],g1[10],p2[10],g2[10]);
89 pro_gen2 prop10(p1[9],p1[11],g1[9],g1[11],p2[11],g2[11]);
90 pro_gen2 prop11(p1[10],p1[12],g1[10],g1[12],p2[12],g2[12]);
91 pro_gen2 prop12(p1[11],p1[13],g1[11],g1[13],p2[13],g2[13]);
92 pro_gen2 prop13(p1[12],p1[14],g1[12],g1[14],p2[14],g2[14]);
93 pro_gen2 prop14(p1[13],p1[15],g1[13],g1[15],p2[15],g2[15]);
94
95 // 3 level
96 gen pr1(p2[4],g0[0],g2[4],g3[4]);
97 gen pr2(p2[5],g1[1],g2[5],g3[5]);
98 gen pr3(p2[6],g2[2],g2[6],g3[6]);
99 gen pr4(p2[7],g2[3],g2[7],g3[7]);
100 pro_gen2 pr5(p2[4],p2[8],g2[4],g2[8],p3[8],g3[8]);
101 pro_gen2 pr6(p2[5],p2[9],g2[5],g2[9],p3[9],g3[9]);
102 pro_gen2 pr7(p2[6],p2[10],g2[6],g2[10],p3[10],g3[10]);

```

```

103 pro_gen2 pr8(p2[7],p2[11],g2[7],g2[11],p3[11],g3[11]);
104 pro_gen2 pr9(p2[8],p2[12],g2[8],g2[12],p3[12],g3[12]);
105 pro_gen2 pr10(p2[9],p2[13],g2[9],g2[13],p3[13],g3[13]);
106 pro_gen2 pr11(p2[10],p2[14],g2[10],g2[14],p3[14],g3[14]);
107 pro_gen2 pr12(p2[11],p2[15],g2[11],g2[15],p3[15],g3[15]);
108
109 //4 level
110 gen po1(p3[8],g0[0],g3[8],g4[8]);
111 gen po2(p3[9],g1[1],g3[9],g4[9]);
112 gen po3(p3[10],g2[2],g3[10],g4[10]);
113 gen po4(p3[11],g2[3],g3[11],g4[11]);
114 gen po5(p3[12],g3[4],g3[12],g4[12]);
115 gen po6(p3[13],g3[5],g3[13],g4[13]);
116 gen po7(p3[14],g3[6],g3[14],g4[14]);
117 gen po8(p3[15],g3[7],g3[15],g4[15]);
118
119 //sum
120 assign Sum[0] = p0[0];
121 sum s1(p0[1],g0[0],Sum[1]);
122 sum s2(p0[2],g1[1],Sum[2]);
123 sum s3(p0[3],g2[2],Sum[3]);
124 sum s4(p0[4],g2[3],Sum[4]);
125 sum s5(p0[5],g3[4],Sum[5]);
126 sum s6(p0[6],g3[5],Sum[6]);
127 sum s7(p0[7],g3[6],Sum[7]);
128 sum s8(p0[8],g3[7],Sum[8]);
129 sum s9(p0[9],g4[8],Sum[9]);
130 sum s10(p0[10],g4[9],Sum[10]);
131 sum s11(p0[11],g4[10],Sum[11]);
132 sum s12(p0[12],g4[11],Sum[12]);
133 sum s13(p0[13],g4[12],Sum[13]);
134 sum s14(p0[14],g4[13],Sum[14]);
135 sum s15(p0[15],g4[14],Sum[15]);
136 assign cout= g4[15];
137 endmodule
138
139

```

Listing 1: 1st problem code

1.0.2 Verilog Testbench Code

```

1 // 16 bit kogge stone adder testbench
2
3 module tb_kogge;
4     reg [15:0] ta, tb;
5     reg tcin;
6     wire [15:0] ts;
7     wire tcout;
8     initial begin
9         $dumpfile("dump.vcd");
10        $dumpvars(0, tb_kogge);
11    end
12
13    koggestone16 final (

```

```
14     .A(ta),
15     .B(tb),
16     .Cin(tcin),
17     .Sum(ts),
18     .cout(tcout)
19 );
20
21 initial
22     begin
23
24         ta[15:0] = 16'b1111110000000000; // 0
25         tb[15:0] = 16'b1000000000000001; // 32769
26         tcin = 1'b0;
27         #5
28         $display("Sum is %b Cout is %b", ts,tcout);
29         #5
30         ta[15:0] = 16'b1000000000000001; // 32769
31         tb[15:0] = 16'b0100000000000001; // 16385
32         tcin = 1'b0;
33         #5
34         $display("Sum is %b Cout is %b", ts,tcout);
35         #5
36         ta[15:0] = 16'b1000000000000011; // 32769
37         tb[15:0] = 16'b1100000000000001; // 16385
38         tcin = 1'b0;
39         #5
40         $display("Sum is %b Cout is %b", ts,tcout);
41         #5
42         $finish;
43     end
44 endmodule
45
46
47
```

Listing 2: 1st problem code

2 Outputs

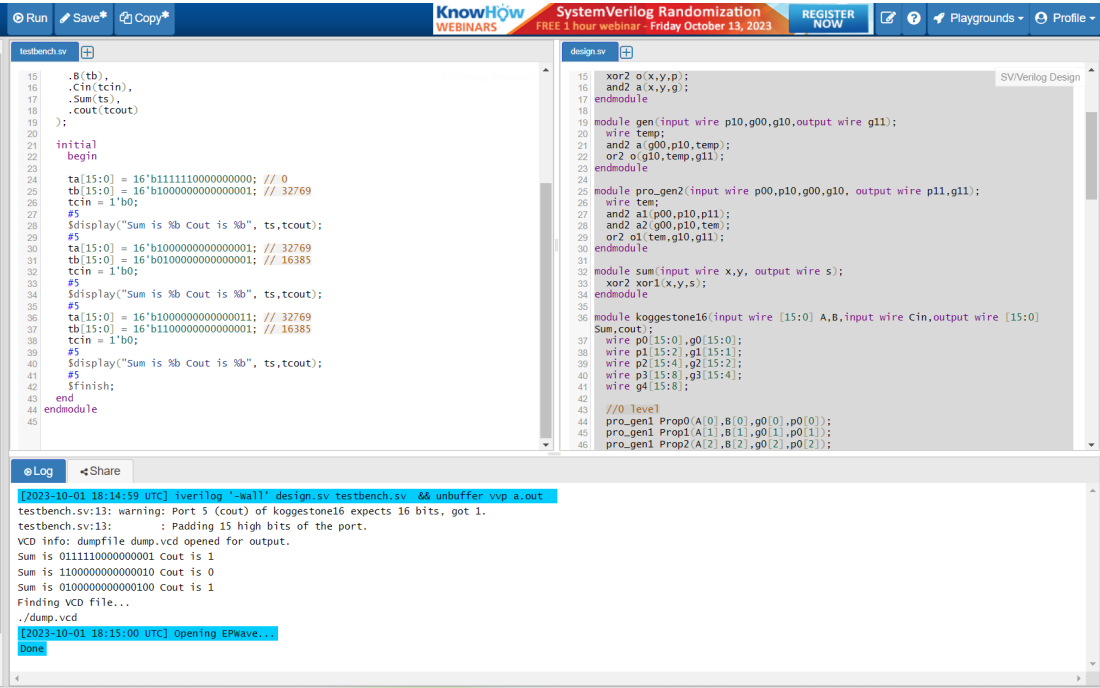


Figure 3: Output in the terminal

 


Figure 4: Output Waveform

3 References

Wikipedia
Youtube